2023 Digital IC Design Homework 4

NAME	莫寶琳				
Student ID F64081169					
Simulation Result					
Functional simulation 100				Gate-level simulation	100
VSM2 > run -ali START!!! Simulation Start Layer 0 output is correct! Layer 1 output is correct! S U M M A R Y Congratulations! Layer 0 data have been generated successfully! The result is FASS!! Congratulations! Layer 1 data have been generated successfully! The result is FASS!! terminate at 46087 cycle """ Mote: Sfinish : C:/Users/user/Desktop/file/testfixture.v(178) Time: 2304350 ns Iteration: 0 Instance: /testfixture 1 Break in Module testfixture at C:/Users/user/Desktop/file/testfixture.v line 178			Threspot		
Synthesis Result					
Total logic elements			554		
Total memory bits			0		
Embedded multiplier 9-bit elements			0		
Total cycle used			46087		
Flow Summary					
< <filter>></filter>					
Flow Status		Suc	Successful - Thu May 18 02:20:05 2023		
Quartus Prime Version		20.1.1 Build 720 11/11/2020 SJ Lite Edition			
Revision Name		ATCONV			
Top-level Entity Name		ATCONV			
Family		Cyclone IV E			
Device		EP4CE55F23A7			
Timing Models		Fina	Final		
Total logic elements		554 / 55,856 (< 1 %)			
Total registers		131	131		
Total pins		82	82 / 325 (25 %)		
Total virtual pins		0	0		
Total memory bits		0/	0 / 2,396,160 (0 %)		
Embedded Multiplier 9-bit elements 0		0/	0/308(0%)		
Total PLLs		0/	0/4(0%)		
Description of your design					

我將電路設計成 4 個 state , 分別為 IDLE,LAYER_0,LAYER_1,FINISH。以下是這四個 state 的行為:

IDLE:讀 Ready 訊號,將 busy 設為 1,指定對 layer0 Mem 做 write 操作,進入 LAYER 0。

LAYER_0:一個 pixel 需要做 10 個 cycle, 共做 64*64 pixels,用>>操作來完成 kernel 小數乘法,由於 kernel 中間為 1,最後再將中間的值(正數)與周圍八個 小數乘法後的值做相減,來符合周圍八個值負數的想法。最後與 bias(-0.75)做 相加,判斷第 13 位是否為 1,是的話代表負數,RELU 後等於 0,不是的話等於原本的值。

因為不想浪費 register 去存 padding 的值,所以我有額外做 Padding case 的判斷。每次做一個 pixel 的 convolution 動作,需要存取原圖 9 個 pixels 的值,所以我 9 個位置都有根據不同的邊緣 case、一般 case 以 iaddr 為變數推公式。

LAYER_1: 一個 pixel 需要做 5 個 cycle, 共做 32*32 pixels,用一個 max_value 來存最大值,前四次依序讀取 layer0(csel = 0,crd = 1,cwr = 0)的值並 更新 max_value,最後一次要將 max_value 無條件進位後存入 layer1(csel = 1,crd = 0,cwr = 1)。

位置的公式我用 current 與 address 去計算,current 每回+2 再%64 代表目前在64 pixel 第幾直行。Address 為做到 32*32 的 layer1 的第幾個 pixel。

公式如下:

左上: current + (address >> 5 << 7)

右上: current + 1 + (address >> 5 << 7)

左下: current +64+ (address >> 5 << 7)

右下: current +65+ (address >> 5 << 7)

無條件進位我的寫法是:判斷最右邊四位是否大於 0?是的話就 $\max_{value+16-max_value[3:0]}$ 。

FINISH:將 busy 設為 0,等待輸出。

 $Scoring = (Total\ logic\ elements + Total\ memory\ bits + 9*Embedded\ multipliers\ 9-bit\ elements)\ X\ Total\ cycle\ used$

* Total logic elements must not exceed 1000.